

Header






Lab Number: 1

Lab Name: An Introduction to SystemVerilog & Digital Components

Task 1:

1.

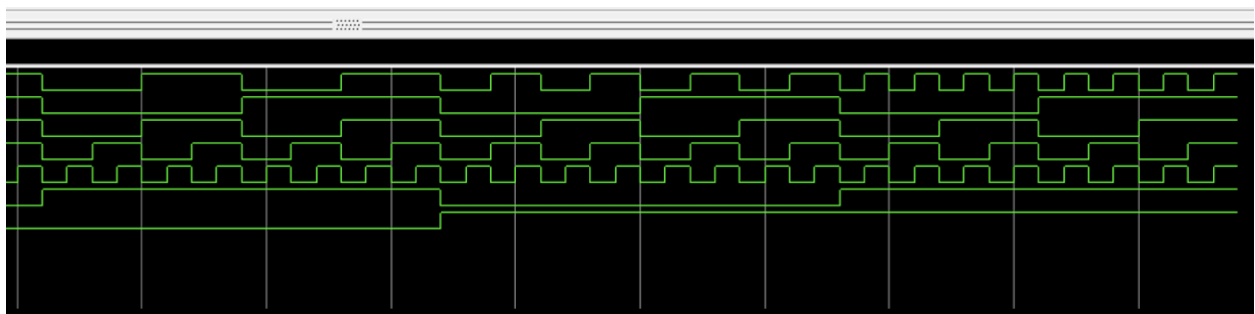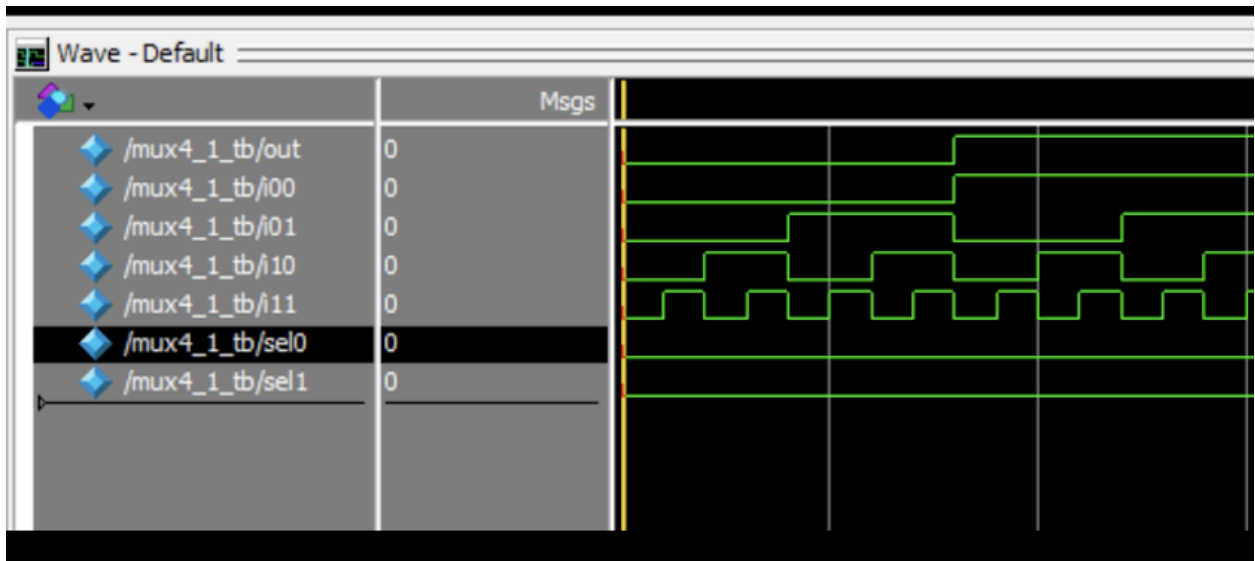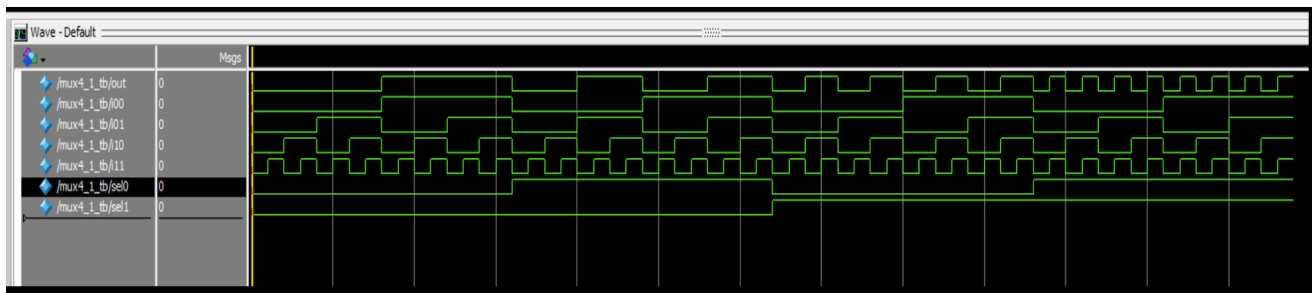


Waveform explanation (Demo)

1. When $sel0 = 0$, $m0$ chooses $i00$ to output, $m1$ chooses $i10$ (i0 input from $mux4-1$ code). Vice-versa when $sel1 = 1$
2. When $sel1 = 0$, m chooses $m0$ output, $m1$ output when $sel1 = 1$

2.

Task 1
2.

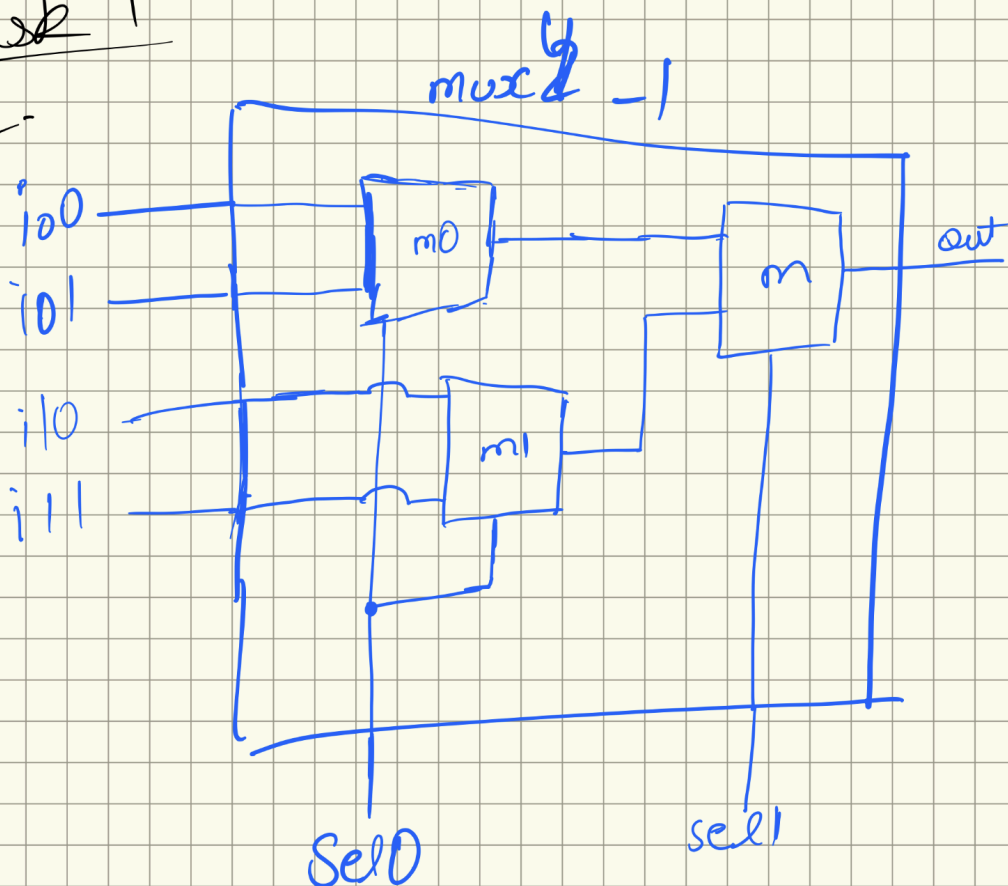

Task 2:

1. One = On, Zero = Off
2. Up = True, Down = False
3. Pressed = True

This lab took me 5 hours to complete